

Part 1: Boolean Simplification

Question 1:

$$\text{EQ1: } AB'C + A'BC' + A'B'C$$

$$\text{EQ2: } ABC + AB'C + A'BC' + A'B'C$$

Simplifying EQ1: $A'B + AB'C + ABC'$

$$B'C(A+A') + A'BC'$$

$$B'C1 + A'BC'$$

$$B'C + A'BC'$$

Simplifying EQ2: $A'B + ABC + ACD' + BCD$

$$B(AC + A') + ACD' + BCD$$

$$B(C + A') + ACD' + BCD$$

$$BC + BA' + ACD' + BCD$$

$$BC + BA' + ACD'$$

Question 2

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Sum of Products (SOP) Form:

Product of Sums (POS) Form:

Part 2: 3-input Boolean Circuit Simplification using Laws

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

POS expression: $(A+B+C)(A+B'+C')(A'+B+C)$


Simplified expression: $AC+BC'+CB'$



```

module Part_1(
    input A,
    input B,
    input C,
    input D,
    output F,
    output FS
);

    assign F = (~A&~B&C&~D) | (~A&B&C&~D) | (~A&B&C&D) | (A&~B&C&~D);
    assign FS = (~A&C&B) | (C&~D&~B) | (C&~D&~A);
endmodule

```

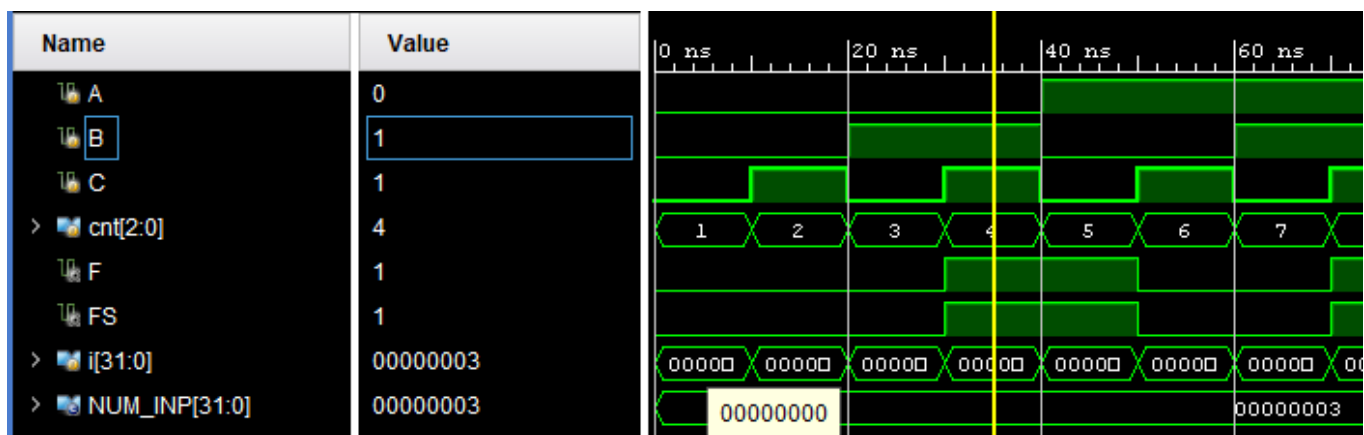

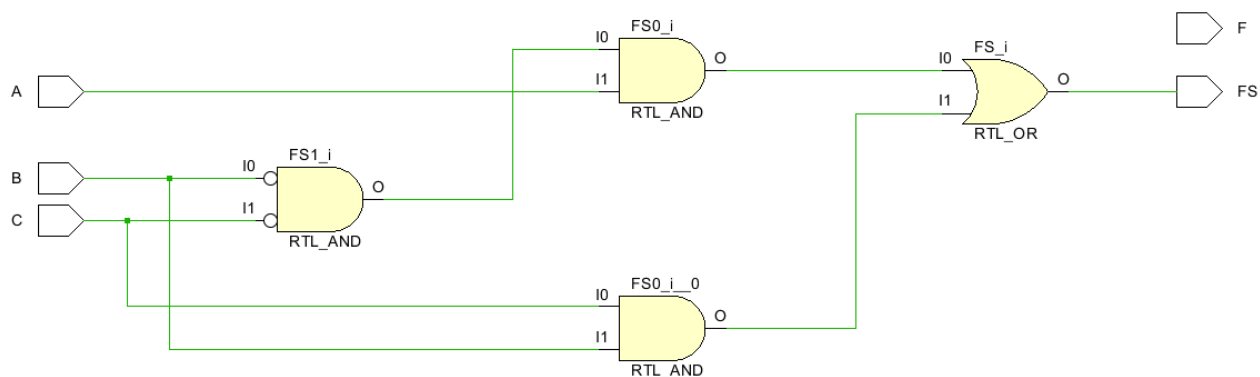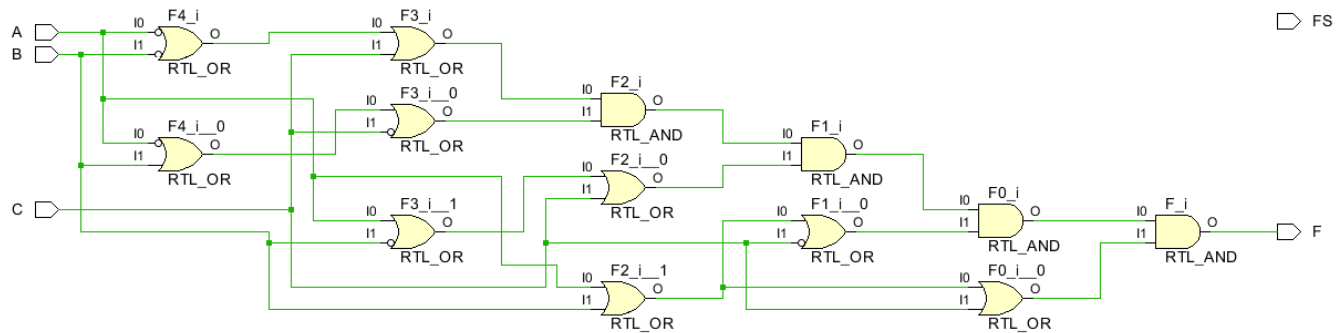

Part 3: 4-input Boolean Circuit Simplification using Laws

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1

A	B	C	D	F
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

Original expression: $A'B'CD' + A'BCD' + A'BCD + AB'CD'$


Simplified expression:



```

module Part_1(
    input A,
    input B,
    input C,
    output F,
    output FS
);

    assign F = (~A|~B|C) & (~A|B|~C) & (A|~B|C) & (A|B|~C) & (A|B|C);
    assign FS = (~B&~C&A) |(C&B);
endmodule

```

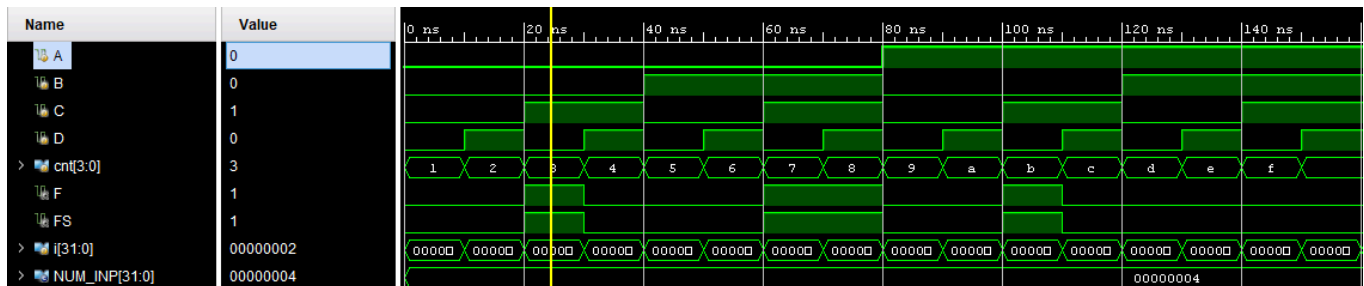

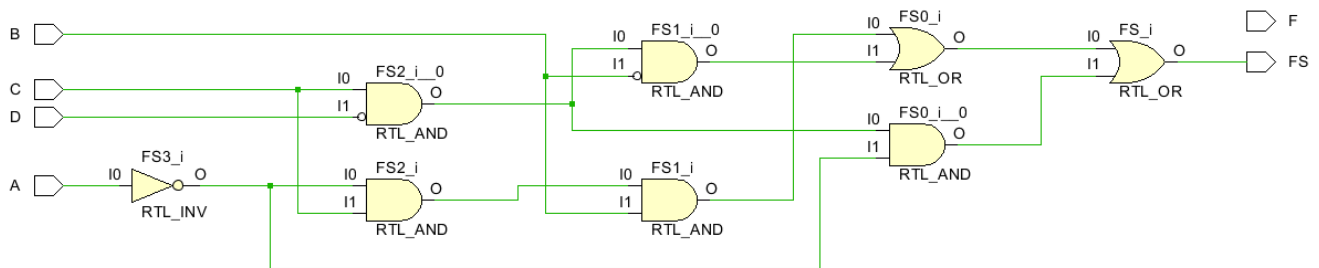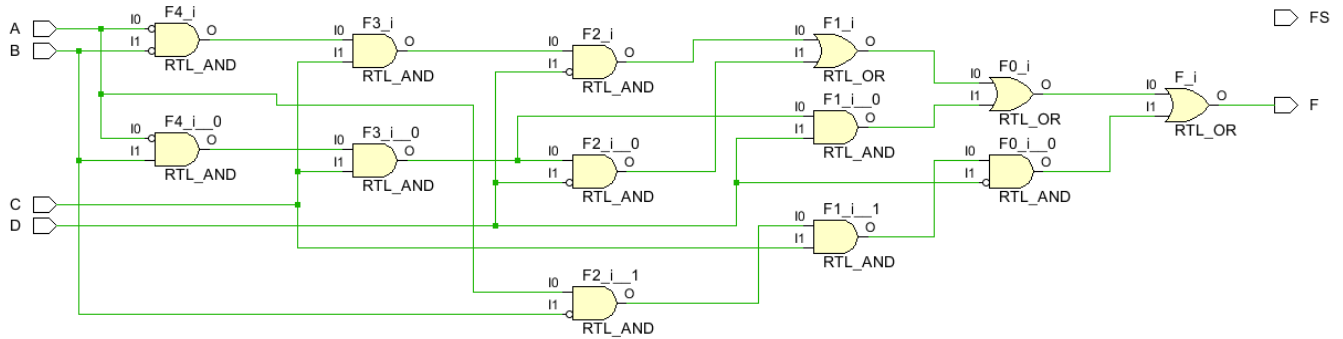

Part 4: Boolean Simplification using K-Maps (Get equation -> Make circuit)

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1



A	B	C	D	F
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0


```

module Part_1(
    input A,
    input B,
    input C,
    input D,
    output FPOS,
    output FSOP
);

    assign FPOS = (~A|~B|~C) & (C|A|B) & (C|A|D) & (~D|B) & (~D|~C);
    assign FSOP = (~A&C&~D) | (A&~B&~D) | (B&~C&A) | (B&~C&D);
endmodule

```

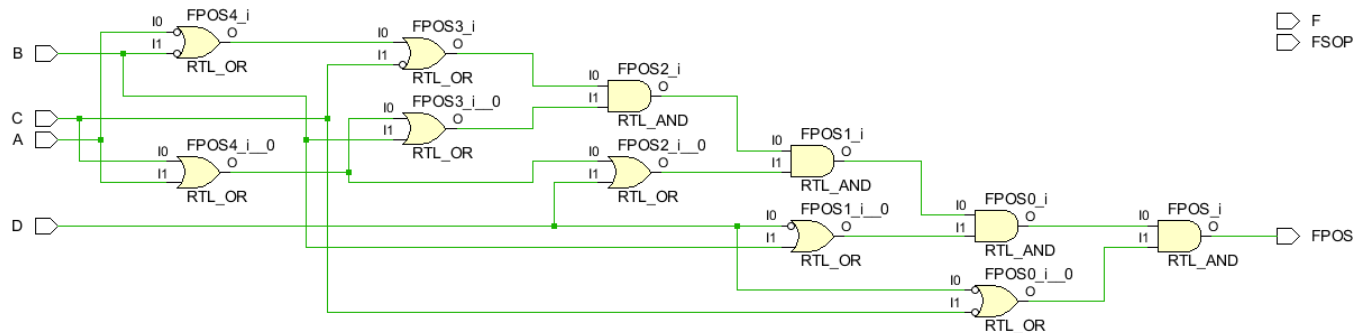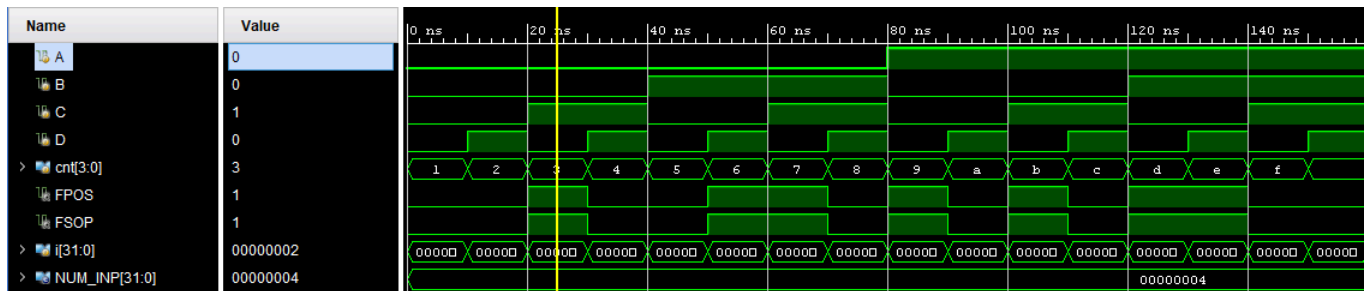

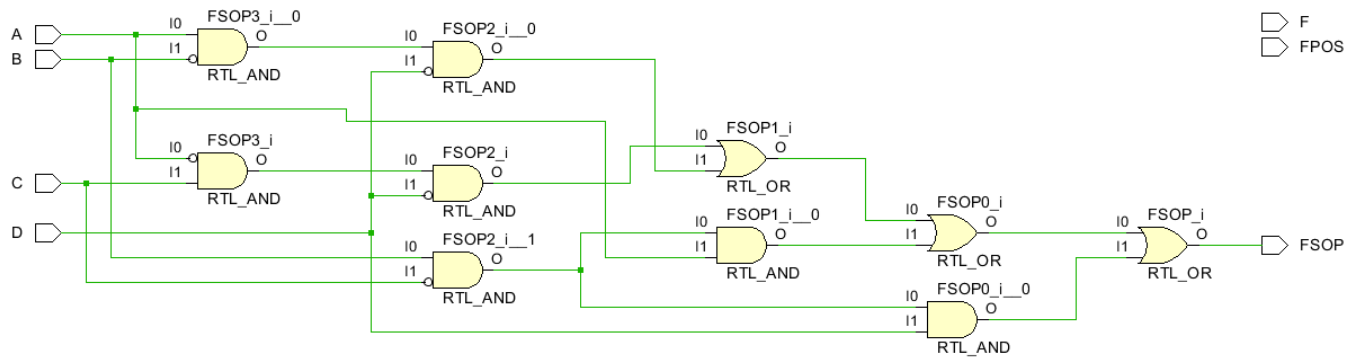

K-Map:

CD\AB	00	01	11	10
00	0	0	0	1 ∨
01	0	1 ∨	0	1 ∧
11	1 ->	<- 1 ∧	0	0
10	<- 1	0	0	1 ->

Overall Deliverables and Q&A

What form of Boolean equations is an ANDs of ORs?

- Product of Sums (POS)

What form of Boolean equations is an ORs of ANDs?

- Sum of Products (SOP)

How many logic gates comprise a 3-variable term?

- A minimum of 2 gates (AND, OR, or NOT) depending on the term.

What does a logic gate represent within the physical realm of computers?

- A logic gate represents a fundamental building block of digital circuits that perform logical operations on binary inputs.